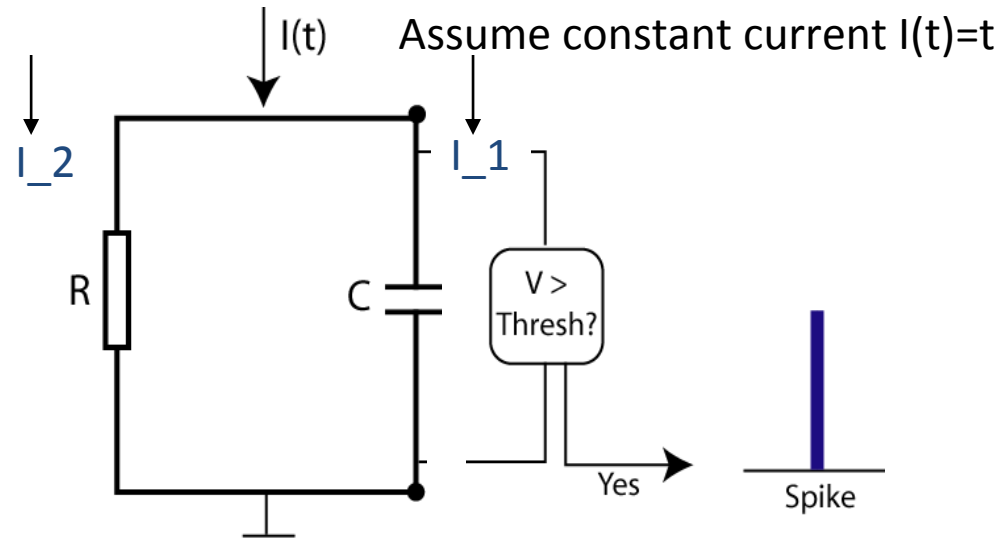


RC Circuit




(1) $C V = Q$ (C capacitance; V voltage; Q charge)

(2) $I_1 = dQ/dt$ (I_1 current)

(3) $C dv/dt = I_1$ (taking derivative in (1) and plugging in (2))

RC Circuit

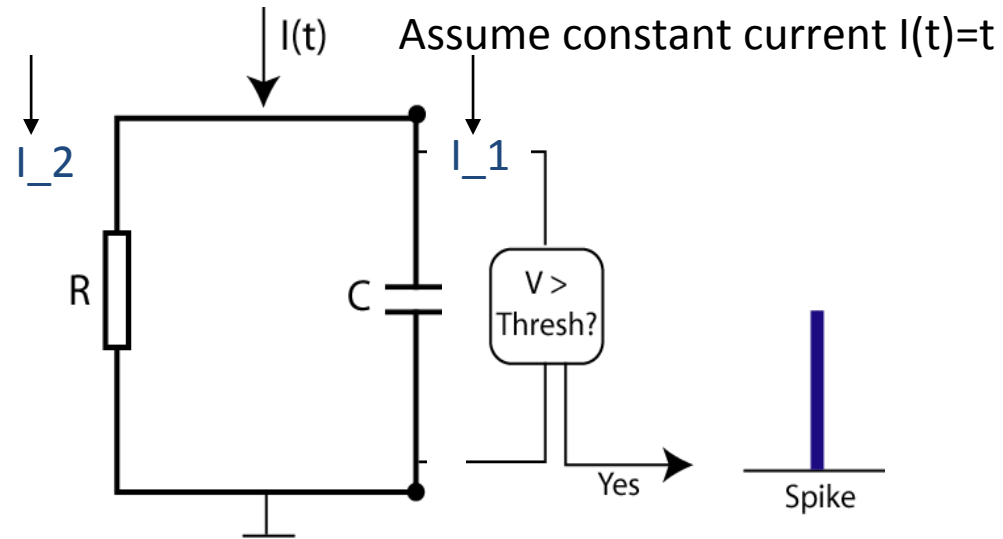

(4) $V = I_2 R$ (Ohms law)

(5) $I_2 = V/R$ (I current)

(6) $I_1 + I_2 = 0$ (Kirchhoff's law)

(7) $-V/R = C dV/dt$ (plugging (3) and (6))

(8) Define $\tau = RC$ (time constant!)

Time constant

Assume constant current $I(t)=I$

$$\tau = RC$$

(1) $Q=CV$

(2) $dQ/dt=I$ (Separable!)
 $Q=It + \text{const}$


(3) $C=Q/V = It/V$

(4) $R=V/I$

(5) $RC = (V/I)(It/V) = t$ (time units!)

[V volt; C Farad; R Ohm; I amper; Q Coulomb]

Leaky Integrate and Fire Circuit

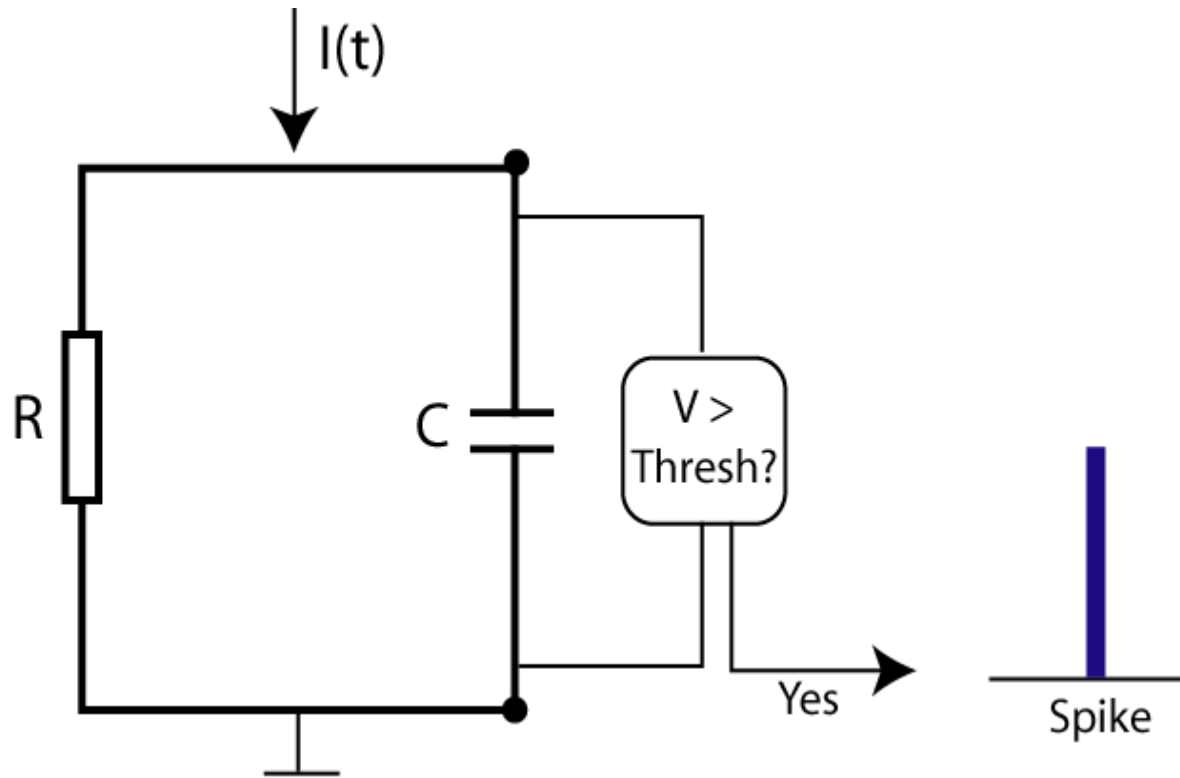

$$C \frac{dv}{dt} = \overset{\text{Leak}}{\frac{-v}{R}} + \overset{\text{Current}}{I(t)}$$